AUDIO ON FPGA

OVERLOOK OF SYSTEM


• The system works to convert the audio in digital form to analog form.

• The audio is a .wav file hence the .wav file format must be taken into consideration when doing the analog to digital conversion.

wav files have 16bit precision meaning it has 65536 quantisation levels.

The nexys A7 uses PWM as a way to output audio .

- In converting the binary to PWM, we use a counter to count from 0 to 65535 to represent the quantisation levels of the .wav file for each 16bit sample of the binary data.
- Whenever each count is less than each 16bit sample the PWM output signal is set high. This means that particular sample was quantised at that particular level.
- This serves as the way of modulating the duty cycle of the PWM to output the audio signal.
 - The clock speed of the counter should be 65536 * 700 = 45.875200MHz as we desire the audio to be played at 700Hz which is within the audible range.

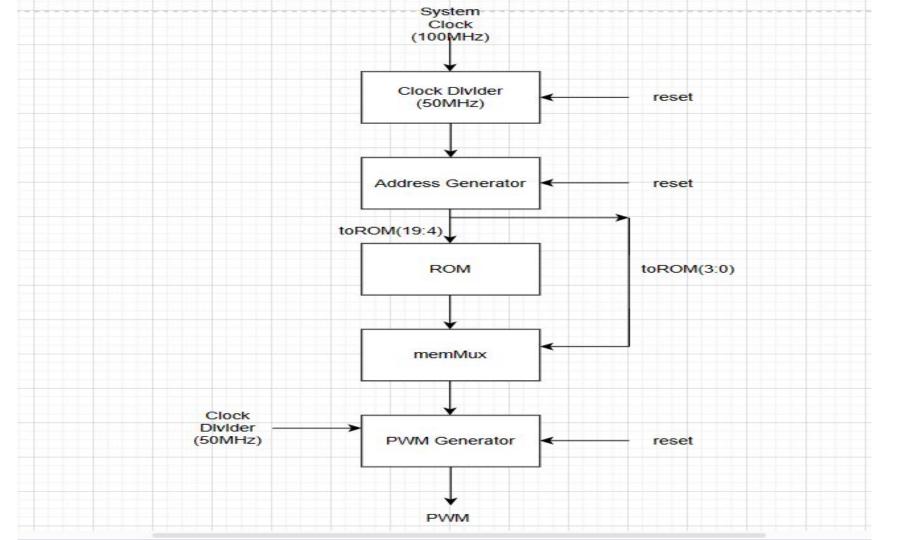

CLOCK DIVIDER

$$\frac{100 \times (10)^6 Hz}{2^x} = 45875200 E$$

$$2^x = \frac{100 \times (10)^6}{45875200}$$

$$2^x = 2.1798$$

$$x = \frac{log 2.1798}{log 2}$$

$$x = 1.1242$$

Therefore a 2 bit counter is used for the clock divider

• Clock divider is to convert the 100MHz clock to 45.875200MHz.

• From the calculations it would take a 2 bit counter to be able to generate about 45.875200MHz clock from the 100MHz clock.

• The exact frequency that would be generated is 50MHz.

Address Generator

• A counter would be used for the address generator.

 The address generator is also used to generate select values for the memory multiplexer.

• The counter counts up to 1048575(20 bits) to address the memory which has a depth of 65536 and width of 256 bits.

 The address would consist of bits 19 downto 4 and the multiplexer select line would be 3 downto 0 of the 20 bit output of the address generator


ROM

The ROM has a depth of 65536 and each address contains 256 bits.

• This memory space contains the audio samples in the binary format.

memMux

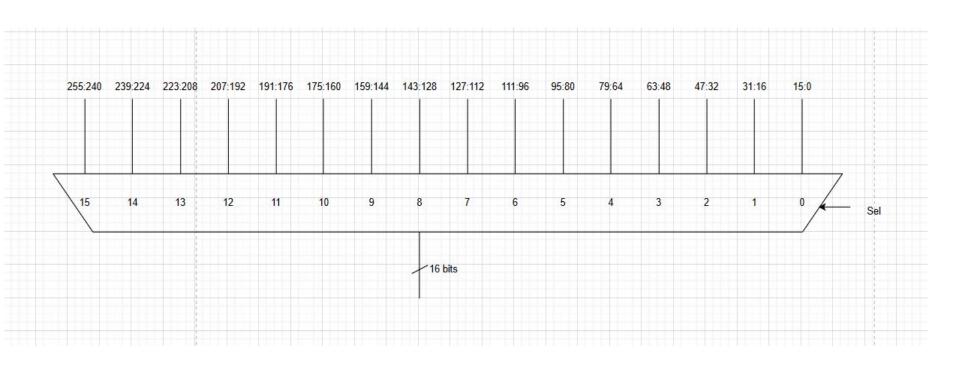This component is a multiplexer for the memory.



PWM GENERATION

